



Homework2 : Ripple Carry Adder

1

- Ripple carry adder
 - ▣ Design a 1_bit full adder using **Dataflow level** Verilog.
 - ▣ Design a four bits ripple carry adder by combining four 1_bit full adders.

